

## 4-bit Arithmetic Logic Unit

Group-3

1505103

1505104

1505106

1505107

1505108

1505109

May 2, 2018

## 1 Designing an ALU

Truth Table : Arithmetic Operations

$cs_2$	$cs_1$	$cs_0$	Arithmetic Operation	$x_i$	$y_i$
0	0	0	Transfer A	$A_i$	0
0	0	1	Increment A	$A_i$	0
0	1	0	Subtraction with Borrow	$A_i$	$\overline{B_i}$
0	1	1	Subtraction	$A_i$	$\overline{B_i}$

Subtract with borrow explanation:

$$\begin{aligned}
 &= A - B - 1 \\
 &= (A + \overline{B} + 1) - 1 \\
 &= A + \overline{B}
 \end{aligned}$$

$$\text{So, } Y = CS_1 \overline{B_i}$$

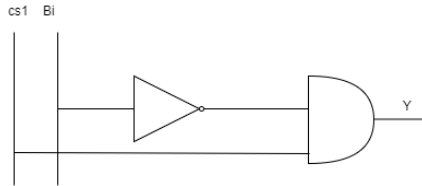


Figure 1:  $Y = CS_1 \overline{B_i}$

## 2 Design of Arithmetic Logic Unit

Truth Table : Logical Operations

$cs_2$	$cs_1$	$cs_0$	$x_i$	$y_i$	$f_i = X_i \oplus Y_i$	Operation
1	0	0	$A_i$	0	$A_i$	OR
1	0	1	$A_i$	0	$A_i + 1$	OR
1	1	0	$A_i$	$B_i$	$A_i - B_i - 1$	AND
1	1	1	$A_i$	$B_i$	$A_i - B_i$	AND

**Explanation:**

we can't modify  $Y_i$  because that would change the arithmetic operations and neither can omit  $A_i$  in any input, So we change  $X_i$ ,

Let,

$$X_i = A_i + K_i$$

$$F_i = X_i \oplus Y_i$$

$$F_i = X_i \oplus 0$$

$$F_i = X_i$$

$$F_i = A_i + K_i$$

But the desired output is  $A_i + B_i$ . So putting  $K_i = B_i$

$$F_i = X_i \oplus Y_i$$

$$F_i = (A_i \oplus K_i) \oplus \overline{B_i}$$

$$F_i = (A_i \oplus K_i)B_i + \overline{(A_i \oplus K_i)}.\overline{B_i}$$

$$F_i = A_iB_i + K_iB_i + \overline{A_i}.\overline{K_i}.\overline{B_i}$$

Here our desired operation is  $A_iB_i$

So,  $A_iB_i + K_iB_i + \overline{A_i}.\overline{K_i}.\overline{B_i} = A_iB_i$

if  $K_i = \overline{B_i}$  Then  $F_i = A_iB_i$

So we need  $K_i = \overline{B_i}$  when we will do OR operation and  $K_i = B_i$  for AND operation.

$CS_2$	$CS_1$	$CS_0$	$B$
1	0	0	$B_i$
1	0	1	$B_i$
1	1	0	$\overline{B_i}$
1	1	1	$\overline{B_i}$

So from the truth table we can derive,

$$X_i = A_i + CS_2(\overline{CS_1}.B(CS_0 + \overline{CS_0}) + CS_1.\overline{B_i}(CS_0 + \overline{CS_0}))$$

$$X_i = A_i + CS_2(CS_1 \oplus B_i)$$

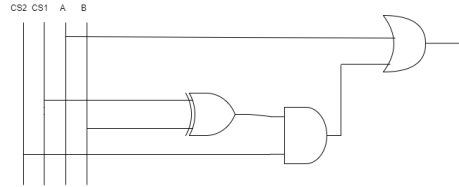


Figure 2:  $X_i = A_i + CS_2(CS_1 \oplus B_i)$

### 3 Final Diagram

$$X_i = A_i + CS_2(\overline{CS_1}.B(CS_0 + \overline{CS_0}) + CS_1.\overline{B_i}(CS_0 + \overline{CS_0}))$$

$$X_i = A_i + CS_2(CS_1 \oplus B_i)$$

$$Y = CS_1\overline{B_i}$$

$$C_{out} = \overline{CS_2}.C_i$$